

Expt. No. 1. VERIFICATION OF OHM'S LAW & KIRCHHOFF'S LAW

1. (a) Verification of ohm's law

Aim:- To Verify ohm's law for a given resistive network

Apparatus Required:


S.NO.	APPARATUS NAME	RANGE	QUANTITY
1.	Dc Regulated Power Supply	(0-30)V	1
2.	Ammeter	(0-200)mA	1
3.	Voltmeter	(0-30)V	1
4.	Resistor	(1K Ω)	1
5.	Rheostat	300 Ω /2A	1
6.	Bread board & Connecting Wires	--	Required

Procedure:

1. Make the connections as per circuit diagram
2. Switch "on" the power supply to RPS and apply a Voltage (say 10V) and take the reading of Voltmeter and ammeter.
3. Adjust the rheostat in steps and take down the readings of ammeter and voltmeter.
4. Plot a graph will be with V along X-axis and I along Y-axis.
5. The graph will be a straight line which verifies ohm's law.
6. Determine the slope of the V-I graph. The reciprocal of the slope gives resistance of the wire.

Result:- Thus the ohm's law is verified for the given circuit.

Circuit Diagram

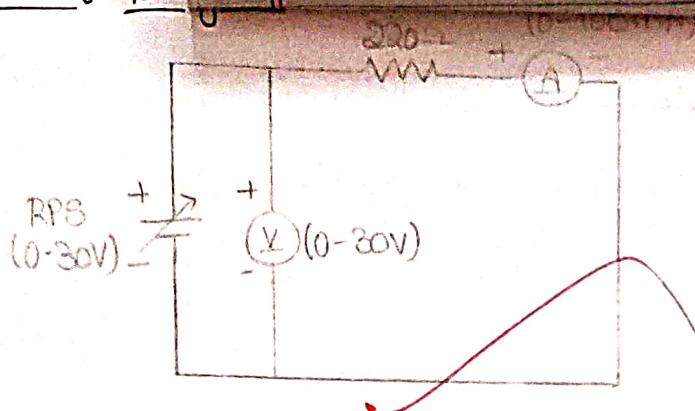

Observations


Resistance = 220Ω

S.No	Voltage (V)	Current (mA)	Resistance (Ω)
1	3	16.5	181.8
2.	6	32	181.5
3.	9	47.5	189.4

$$\text{Average } R = \frac{R_1 + R_2 + R_3}{3} \Rightarrow R = \frac{181.8 + 181.5 + 189.4}{3} = \frac{558.7}{3}$$

$$\text{Average } R = 186.2 \Omega$$


Model Graph

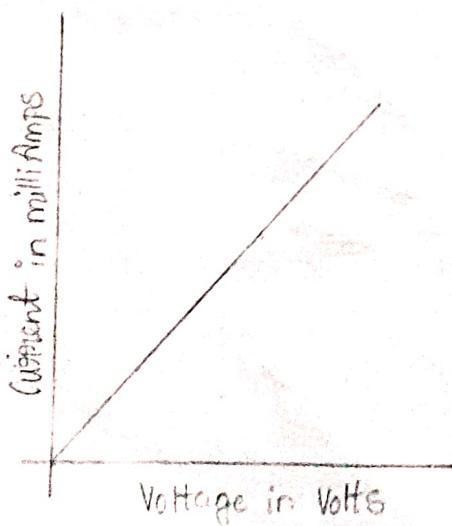


Theoretical calculation	20	20
Observation	20	20
Execution of Practice	30	30
Viva	10	9
Record	20	20
Total Score	100	99
Date of Experiment	29/01/2025	
Date of record	29/01/2025	
Submission	Faculty Signature	

Y₀₀₁₁₂ = 10 m/s + 0.4 m

X₀₀₁₁₂ = 10 m/s + 16.5 cm/s

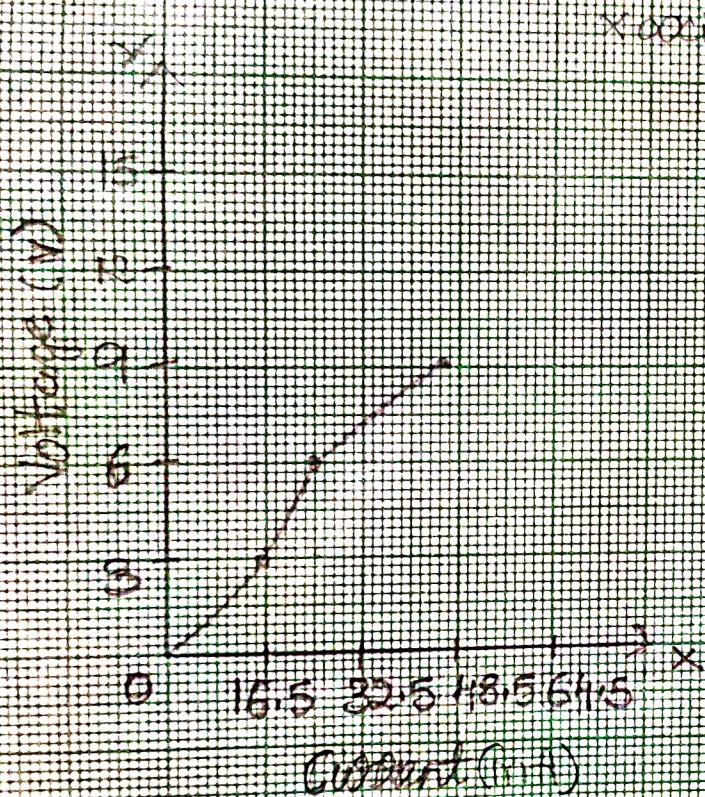

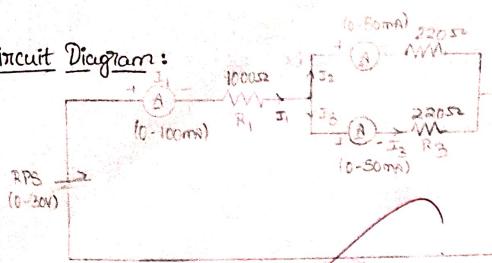Circuit Diagram:KCL - Theoretical Values

Sl. No.	Voltage (E)	Current			$I_1 = I_2 + I_3$
		I_1 mA	I_2 mA	I_3 mA	
1.	5	0.005	2.5×10^{-3}	2.5×10^{-3}	0.005
2.	10	0.01	5×10^{-3}	5×10^{-3}	0.01
3.	15	0.015	7.5×10^{-3}	7.5×10^{-3}	0.015

KCL - Practical Values

Sl. No.	Voltage (E)	Current			$I_1 = I_2 + I_3$
		I_1 mA	I_2 mA	I_3 mA	
1.	5	4	2	2	4
2.	10	8	4	4	8
3.	15	12	6	6	12

Calculations

• 5 Volts
 $I_1 = V/R = 5/1000 = 5 \times 10^{-3} A \rightarrow I_2 = 5/220 = 2.5 \times 10^{-3} A$

• 10 Volts
 $I_1 = V/R = 10/1000 = 0.01 A \rightarrow I_2 = 10/220 = 5 \times 10^{-3} A$

• 15 Volts
 $I_1 = V/R = 15/1000 = 0.015 A \rightarrow I_2 = 15/220 = 7.5 \times 10^{-3} A$

1. (b) Verification of Kirchhoff's Current law

Aim: To Verify Kirchhoff's Current law for the given Circuit

Apparatus Required:-

S.No	APPARATUS NAME	RANGE	QUANTITY
1.	DC Regulated power Supply	(0-30)V	1
2.	Ammeter	(0-100)mA	3
3.	Resistor	470Ω, 330Ω	2
4.	Bread board & Connecting wires	--	Required

Statement:

KCL: The algebraic sum of the currents meeting at a node junction is equal to zero.

Procedure:


- Give the connections as per the Circuit diagram
- Set a particular value in RPS
- Note down the corresponding ammeter reading
- Repeat the same for different voltages

Marks Obtained:

Theoretical Calculations	20	✓
Observation	20	✓
Execution of Practice Examples	30	10
Viva	10	9
Record	20	20
Total Score	100	99
Date of Experiment	09/11/2025	
Date of record	2nd Nov	
Submission	Faculty Signature	

Result: Thus the Kirchhoff's Current law is verified for a given circuit

Circuit Diagram

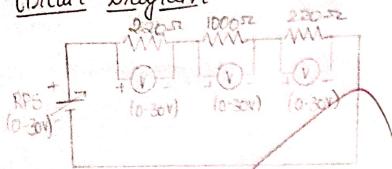

KVL - Theoretical Values

S.No	RPS Voltage V	V ₁	V ₂	V ₃	KVL = V = V ₁ + V ₂ + V ₃
1.	5	0.7634	3.47	0.7634	4.99
2.	10	1.5268	6.94	1.5268	9.99
3.	15	2.288	10.4	2.288	14.97

KVL - Practical Values

S.No	RPS Voltage V	V ₁	V ₂	V ₃	KVL = V = V ₁ + V ₂ + V ₃
1.	5	0.5	3	0.5	4
2.	10	1	6	1	8
3.	15	1.5	9	1.5	12

Calculations

$$R_{eq} = 220 + 1000 + 220 = 1440 \Omega$$

$$I_1 = \frac{5}{1440} = 3.47 \text{ mA}, I_2 = \frac{10}{1440} = 6.94 \text{ mA}$$

$$I_3 = \frac{15}{1440} = 10.4 \text{ mA}$$

• 5 volt

$$V_1 = 3.47 \times 10^{-3} \times 220 = 0.7634 \text{ V}$$

$$V_2 = 6.94 \times 10^{-3} \times 1000 = 6.94 \text{ V}$$

$$V_3 = 10.4 \times 10^{-3} \times 220 = 0.7634 \text{ V}$$

10 volt

• 10 volt

$$V_1 = 6.94 \times 10^{-3} \times 220 = 1.5268 \text{ V}$$

$$V_2 = 6.94 \times 10^{-3} \times 1000 = 6.94 \text{ V}$$

$$V_3 = 6.94 \times 10^{-3} \times 220 = 1.5268 \text{ V}$$

15 volt

$$V_1 = 10.4 \times 10^{-3} \times 220 = 2.288 \text{ V}$$

$$V_2 = 10.4 \times 10^{-3} \times 1000 = 10.4 \text{ V}$$

$$= 2.288 \text{ V}$$

Page No.

1. (a) Kirchhoff's Voltage law

Aim: To Verify Kirchhoff's Voltage law for the given Circuit.

Apparatus Required:

S.No	APPARATUS NAME	RANGE	QUANTITY
1.	Dc Regulated Power Supply	(0-30)V	2
2.	Voltmeter	(0-30)V	3
3.	Resistor	1KΩ, 200Ω, 330Ω	Each one
4.	Bread board & Connecting wires	--	Required

Statement:

KVL: In any closed path / mesh, the algebraic sum of all voltages is zero.


Procedure:

- Give the connections as per the circuit diagram.
- Set a particular value in RPS
- Note all the voltage reading
- Repeat the same for different voltages.

Marks obtained

Theoretical Calculations	20	20
Observation	20	20
Execution of Backie Scans	30	30
Viva	10	7
Record	20	20
Total Score	100	99
Date of Experiment		30/01/2025
Date of Record		
Submission		Faculty signature

Result: Thus Kirchhoff's Voltage law is verified for the given circuit.

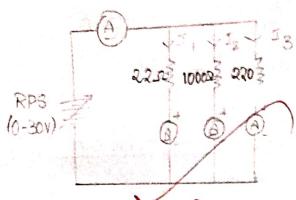Circuit DiagramObservations

S.No	Voltage (V)	Current (mA)			
		I_1	I_2	I_3	I_t
1	5	21	4	21	46
2	10	44	6	44	98

Expt-No.2: VERIFICATION OF CURRENT AND VOLTAGE DIVISION RULES

Aim: To calculate the individual branch currents and total current drawn from the power supply using Current and Voltage division rules

Apparatus Required:

S.No	APPARATUS NAME	RANGE	QUANTITY
1.	DC Regulated Supply	(0-30)V	1
2.	Ammeter	(0-200)mA	4
3.	Resistor	1KΩ-220Ω	Each two
4	Bread board and Connecting wires	--	Required


Procedure:

1. Give the connections as per the circuit diagram
2. Set a particular value in RPS.
3. Note down the corresponding ammeter reading
4. Repeat the same for different voltages

Marks Obtained:

Theoretical Calculations	20	20	
Observation	20	20	
Execution & Practice Example	30	30	
Viva	10	9	
Record	20	20	
Total Score	100	99	
Date of Experiment			30/11/2025
Date of Record Submission			20/12/2025


Result: Thus the individual branch currents and total current drawn from the power supply are calculated using Current and Voltage division

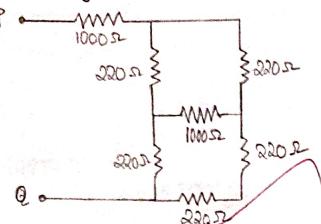Circuit DiagramObservation

S.No	Theoretical Value (R _{PQ}) in Ohm	Measured Value (R _{PQ}) in ohm
1	1.2 kΩ	1.4 kΩ

Calculation

(i) Delta - Star transformation

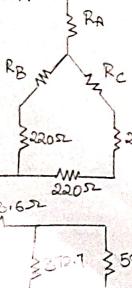

$$R_A = \frac{R_{AB} R_{CA}}{R_{AB} + R_{BC} + R_{CA}} = \frac{220 \times 220}{220 + 1000 + 220} = \frac{48400}{1440} = 33.61 \Omega$$

$$R_B = \frac{R_{AB} + R_{BC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{220 + 1000}{1440} = \frac{220000}{1440} = 152.7 \Omega$$

$$R_C = \frac{R_{CA} + R_{BC}}{R_{AB} + R_{BC} + R_{CA}} = \frac{220 + 1000}{1440} = \frac{220000}{1440} = 152.7 \Omega$$

$$R_{eq} = \frac{592.7 \times 312.7}{592.7 + 312.7} = \frac{920899.29}{965.4} = 228.8 \Omega$$

$$R_{eq} = 1033.6 + 228.8 = 1262.4 \Omega = 1.2 \text{ k}\Omega$$

Expt. No.

3. VERIFICATION OF STAR DELTA TRANSFORMATION

Aim: To calculate the equivalent circuit resistance Using Star delta transformation technique

Apparatus Required:-

S.No	Apparatus Name	Range	Quantity
1	Resistor		
2	Bread Board & Connecting	--	Required

Procedure:-


- Give the connections as per the circuit diagram
- Determine the Equivalent resistance of the circuit between P and Q Using Star-delta transformation technique
- Verify the same by connecting a multimeter across PQ.

Marks obtained:

Theoretical Calculations	20	12
Observation	20	20
Execution of Practice Examples	30	30
Viva	10	9
Record	20	20
Total Score	100	99
Date of Experiment		30/11/2025
Date of record Submission		

Result:-

Thus the Equivalent circuit resistance is obtained using Star delta transformation technique.

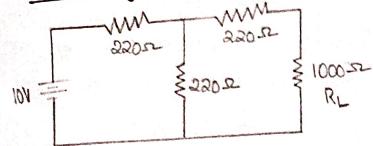Circuit DiagramFind V_{Th}


$$R_{eq} = 220 + 220 = 440\Omega$$

$$I = \frac{V}{R} = \frac{10}{440} = 0.022\text{A}$$

$$V_{oc} = 0.022 \times 220 = 4.84 \rightarrow \text{approx } 5\text{V}$$

Find I_L

$$I_L = \frac{5}{330 + 1000} = \frac{5}{1330} = 3.76\text{ mA}$$

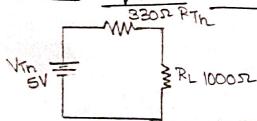Thevenin's Equivalent CircuitObservation:-

S.No	Supply Voltage (V)	Theoretical Values		Measured Values		
		R _{Th} (Ω)	V _{Th} (V)	I _L (mA)	R _{Th} (Ω)	V _{Th} (V)
1	10V	330	5	3.76	320	4.5

Calculation

Thevenin's Theorem:

Find R_{Th}

$$\frac{1}{R_{eq}} = \frac{1}{220} + \frac{1}{220} = \frac{2}{220}$$

$$R_{eq} = \frac{220}{2} = 110\Omega$$

$$R_{eq} = \frac{110 + 220}{2} = 330\Omega$$

$$\therefore 330\Omega \rightarrow R_{Th}$$

$$\therefore 5V - V_{Th}$$

Expt. No. 4. VERIFICATION OF THEVENIN'S AND NORTON'S THEOREM 8

Aim:- To Verify the Equivalent Circuit parameters of Thevenin's and Norton's Theorems

Apparatus Required:-

S.No	Apparatus Name	Range	Quantity
1.	DC Regulated Power Supply	(0-30)V	1
2.	Voltmeter	(0-30)V	1
3.	Ammeter	(0-200)mA	1
4.	Resistor	330Ω, 220Ω	Each two
5.	Multimeter	-	1
6.	Bread Board & Connecting wires		Required

Procedure :- [Thevenin's Theorem]

- Give the connections as per the circuit diagram.
- Measure R_{th} using a multimeter.
- Measure V_{th} across 220Ω (R₂).
- Measure load current I_L through R_L.

Procedure :- [Norton's Theorem]

- Give the connections as per the circuit diagram.
- Measure R_{th} using a multimeter.
- Measure I_N.
- Measure load current I_L through R_L.

Calculation:

Norton's theorem

Find R_N

$$\frac{1}{R_{eq}} = \frac{1}{220} + \frac{1}{220} = \frac{2}{220}$$

$$R_{eq} = \frac{220}{2} = 110\Omega$$

$$R_N = 330\Omega$$

$$R_{eq} = 110 + 220 = 330\Omega$$


Find I_N

$$I_N = 14\text{ mA}$$

Find I_L

$$I_L = \frac{I_N \times R_N}{R_N + R_L} = \frac{14 \times 10^{-3} \times 330}{330 + 1000} = \frac{4.62}{1330} = 3.41\text{ mA}$$

Norton's Equivalent Circuit

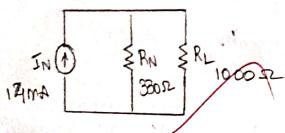Observations

S.No	Supply Voltage (V)	Theoretical Values			Measured Values		
		$R_N(\Omega)$	$I_N(\text{mA})$	$I_L(\text{mA})$	$R_N(\Omega)$	$I_N(\text{mA})$	$I_L(\text{mA})$
1	10 V	330	14	3.41	330	13.5	3.34

Marks obtained:

Theoretical Calculations	20	20
Observation	20	20
Execution of practice Example	30	30
Viva	10	9
Record	20	20
Total Score	100	99
Date of Experiment	1/21/2025	
Date of record		
Submission		

Result :-

Thus the equivalent circuit parameters are obtained using Thevenin's and Norton's theorem.

Expt. No. 05. VERIFICATION OF MAXIMUM POWER TRANSFER THEOREM AND SUPERPOSITION THEOREM

5(a)

Verification of maximum power transfer Theorem

Aim:- To Verify maximum power transfer Theorem


Apparatus Required:

S.NO	APPARATUS NAME	RANGE	QUANTITY
1	Dc Regulated Power Supply	(0-30)V	1
2.	Voltmeter	(0-30)V	1
3	Ammeter	(0-200)mA	1
4	Resistor	$330\Omega, 220\Omega$	Each two
5	Multimeter	-	1
6	Bread Board & Connecting	-	Required

Procedure:-

1. Give the connections as per the circuit diagram.
2. Measure R_{th} using a multimeter
3. Measure V_{th} across 220Ω (R_2)
4. Measure load current I_L through R_L
5. calculate the maximum power transferred to the load

Circuit diagram

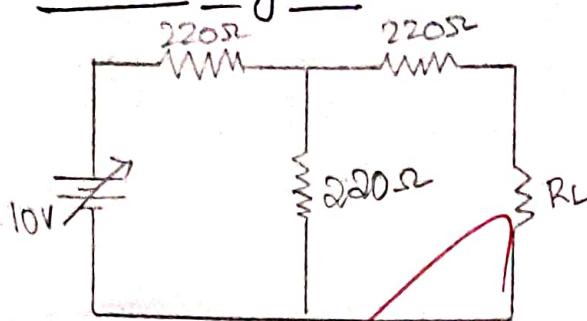


Calculation

Find R_{th} :

$$\frac{1}{R_{th}} = \frac{1}{220} + \frac{1}{220} = \frac{2}{220}$$

$$R_{th} = \frac{220}{2} = 110$$

$$R_{th} = 110 + 220 = 330\Omega$$

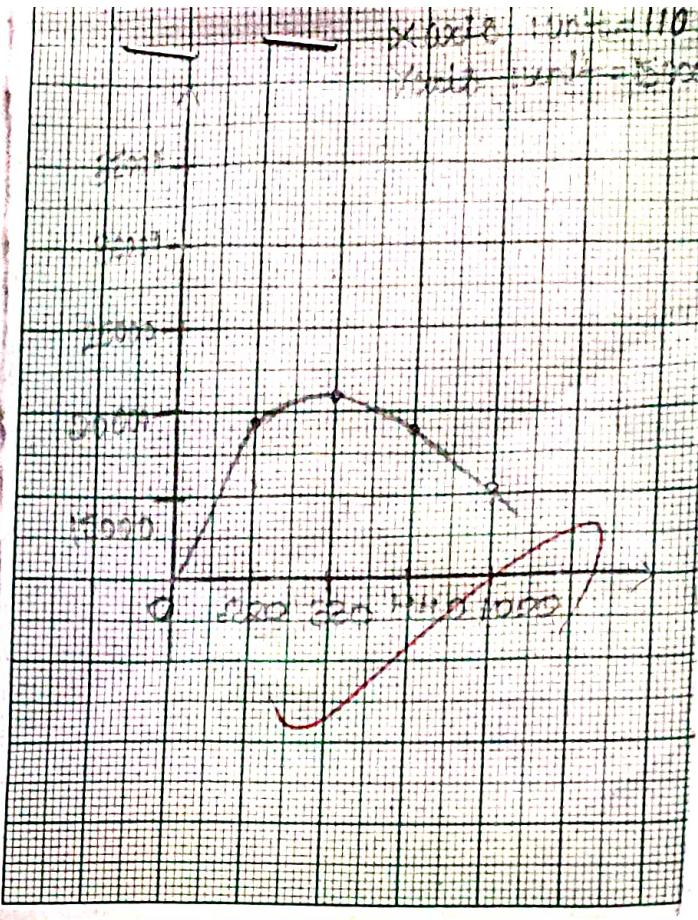

Find I_L :

$$I_L = 8A$$


Find P_{max} :

$$P_{max} = I_L^2 \times R_L = 8 \times 8 \times 330 = 64 \times 330 = 21120 \text{ Watts}$$

Observations

S.No	Supply Voltage (V)	$R_L (\Omega)$	Measured Values		Maximum Power $P_{max} = I^2 R$ (Watts)
			I_L (mA)		
1.	10	220Ω	9.5		19855
2.	10	330Ω	8		21120
3.	10	440Ω	6.5		18590
4.	10	1000Ω	4		16000

Model graph

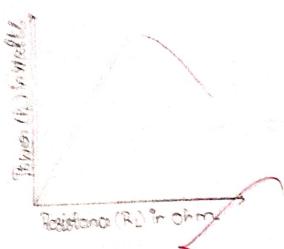

Marks obtained

Theoretical Calculations	20	20
Observation	20	20
Execution of Practice Examples	20	20
Viva	10	?
Record	20	20
Total Score	100	100
Date of Experiment	1/2/2025 99	
Date of record Submission		

Result:

Thus the Maximum power transfer theorem is verified

5(b)

Verification of Superposition Theorem

Aim: To determine the current flow through the load resistor using Superposition Theorem

Apparatus Required:

S.No	Apparatus Name	Range	Quantity
1	Dc Regulated Power Supply	(0-30)V	2
2	Voltmeter	(0-30)V	1
3	Ammeter	(0-200)mA	1
4	Resistor	1k Ω , 220 Ω , 330 Ω	Each one
5	Multimeter	-	1
6	Bread board & Connecting wires	-	Required

Procedure:

1. Give the connections as per the circuit diagram.
2. Measure Current flow through 220 Ω by connecting both the supplies.
3. Short circuit 15V source
4. Measure Current flow through 220 Ω by connecting 20V Supply.
5. Short circuit 20V source
6. Measure current flow through 220 Ω by connecting 15V Supply.
7. Verify the net current through 220 Ω resistor.