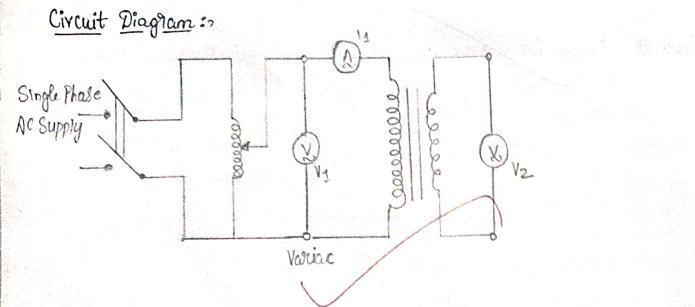


Circuit Diagram :-Tabular Column :-

Sl.No	Primary Voltage ( $V_1$ ) in Volts	Secondary Voltage ( $V_2$ ) in Volts	Primary Current ( $I_1$ ) in ampere	Turn ratio $K = V_2/V_1$	Secondary current $I_2 = I_1/K$
1.	230V	230V	0.21A	1	0.21
2.	230V	228V	0.4A	0.99	0.40
3.	230V	226V	0.6A	0.98	0.61
4.	230V	224V	0.8A	0.97	0.82

Calculations

$$\textcircled{1} \quad K = \frac{230}{230} = 1$$

$$\textcircled{1} \quad I_2 = \frac{0.21}{1} = 0.21$$

$$\textcircled{2} \quad K = \frac{228}{230} = 0.99$$

$$\textcircled{2} \quad I_2 = \frac{0.4}{0.99} = 0.40$$

$$\textcircled{3} \quad K = \frac{226}{230} = 0.98$$

$$\textcircled{3} \quad I_2 = \frac{0.6}{0.98} = 0.61$$

$$\textcircled{4} \quad K = \frac{224}{230} = 0.97$$

$$\textcircled{4} \quad I_2 = \frac{0.8}{0.97} = 0.82$$

2/2/25

Expt : 08 Calculation of Secondary turns and current in a transformer

Aim:- To calculate the Secondary turns and current in a Single phase transformer

Apparatus Required :-

SI.NO	APPARATUS	PINNE	QUANTITY
1	Single Phase transformer	230/115V	1
2	Auto transformer	0-300VAC	1
3	Voltmeter	0-300VAC	1
4	Ammeter	0-10A	1
5	Connecting Wires	-	As required
6	Single Phase AC Power Supply	-	-

Theory:-

It is essential to know the relative polarity at any instant of primary and Secondary terminals for making correct connections. When the two transformers are to be connected in parallel to share the load on the system. The marking is correct if voltage  $V_3$  is less than  $V_1$ , such as polarity is termed as subtractive polarity. The standard practice is to have subtractive polarity. The standard ~~is~~ because it reduces the voltage stress between adjacent loads. In case  $V_3 > V_1$ , the EMF induced in primary and secondary have additive relation and transformer is said to have additive polarity.

Name plate details:-

### KVA Rating

Rated H.V Side Voltage 230 V

Rated H.V Side Current 4.5 A

Rated L.V Side Voltage 230 V

Rated L.V Side current 4.5 A

### Procedure:

1. Connect the circuit as shown in the diagram.
2. Switch on the ac supply
3. Reduce Voltage  $V_1$  across primary and  $V_2$  across
4. If  $V_1 > V_2$  Then transformer is Step down.
5. If  $V_2 > V_1$  then transformer is Step up.
6. switch off ac supply.

### Marks obtained:

Theoretical Calculations	20	20
Observation	20	20
Execution of Practice Examples	30	30
Viva	10	8
Record	20	20
Total Score	100	92
Date of Experiment	20/21/25	
Date of record Submission		Faculty Signature

Result: Thus the secondary turns and current in a single phase ~~thy~~ transformer is calculated.

20/2/25

## Expt 09. Load Test on a Single Phase transformer

Aim: To conduct load test on single phase transformer and to find efficiency and percentage regulation.

## Apparatus Required:

S.NO	APPARATUS	RANGE	TYPE	Q'TY
1	Ammeter	(0-10)A (0-5)A	MI, MI	1, 1
2	Voltmeter	(0-150)V (0-300)V	MI, MI	1, 1
3	Wattmeter	(300V, 5A)(150V, 5A)	MPF, HPF	1
4	Auto Transformer	14, 10-200V	-	1
5	Resistive load	5kW, 230V	-	1
6	Connecting wires	2.5 Sq. mm	Copper	Few

## Precautions:

1. Auto Transformer Should be in minimum position
2. The AC Supply is given and removed from the transformer under no load condition.

## Name plate details:

## • KVA Rating:


- Rated H.V Side Voltage: 230V
- Rated H.V Side Current: 5A
- Rated L.V Side Voltage: 115V
- Rated L.V Side Current: 10A

## Fuse Rating Calculations:




The required fuse ratings for o.c. are 80% of rated current  
on L.V Side =  $(20/100) \times$  Rated current on L.V Side.

The required fuse ratings for s.c. are 120% of rated current on H.V Side.
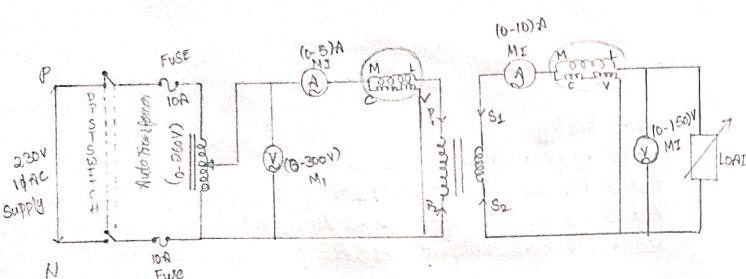
$$\frac{125 \times 5}{100} = 6.25 \text{ A}$$



S.NO	LOAD	Primary			Secondary			INPUT POWER MEASURED	OUTPUT POWER MEASURED	Efficiency %	Regulation %
		V <sub>1</sub>	I <sub>1</sub>	W <sub>1</sub>	V <sub>2</sub>	I <sub>2</sub>	W <sub>2</sub>				
1	NO LOAD	230	0	0	215	0	0	0	0	0	-
2	200	228	1	220	210	1	210	880	880	55	0.9
3	400	226	1.5	270	205	1.5	180	1080	960	29	1.7
4	600	225	2.6	600	205	2.5	170	2400	1540	64	2.8
5	800	224	3.5	800	200	3.1	180	3200	1960	61	2.6

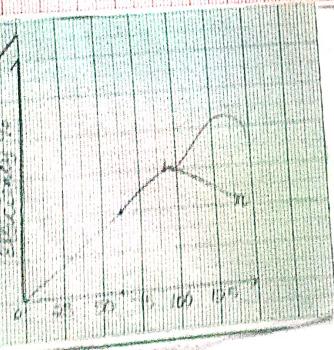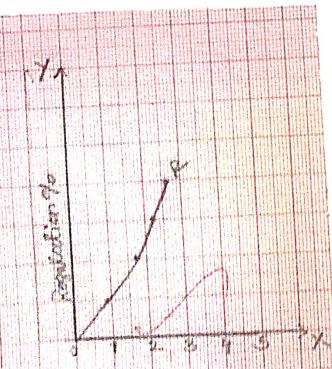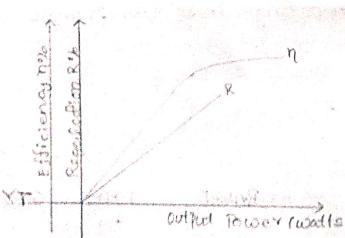**Procedure:**

1. Connections are made as per the circuit diagram
2. After checking the no load condition, minimum position of auto-transformer and DPST switch is closed.
3. Ammeter, Voltmeter and Wattmeter readings on both primary side and secondary side are noted.
4. The load is increased and for each load, voltmeter, ammeter and wattmeter reading on both Primary and Secondary sides are noted.
5. Again no load condition is obtained and DPST switch is opened.

**Formulae:**

$$\text{Output Power} = W_2 \times \text{Multiplication factor}$$


$$\text{Input Power} = W_1 \times \text{Multiplication factor}$$

$$\text{Efficiency } \eta \% = \frac{\text{Output Power}}{\text{Input Power}} \times 100\%$$

**Marks obtained:**

Theoretical Calculations	20	2
Observation	40	20
Execution of Practice Examples	30	20
Viva	10	9
Record	20	20
Total Score	100	99
Date of Experiment	20/2/2025	
Date of Record Submission		Mr. [Signature]

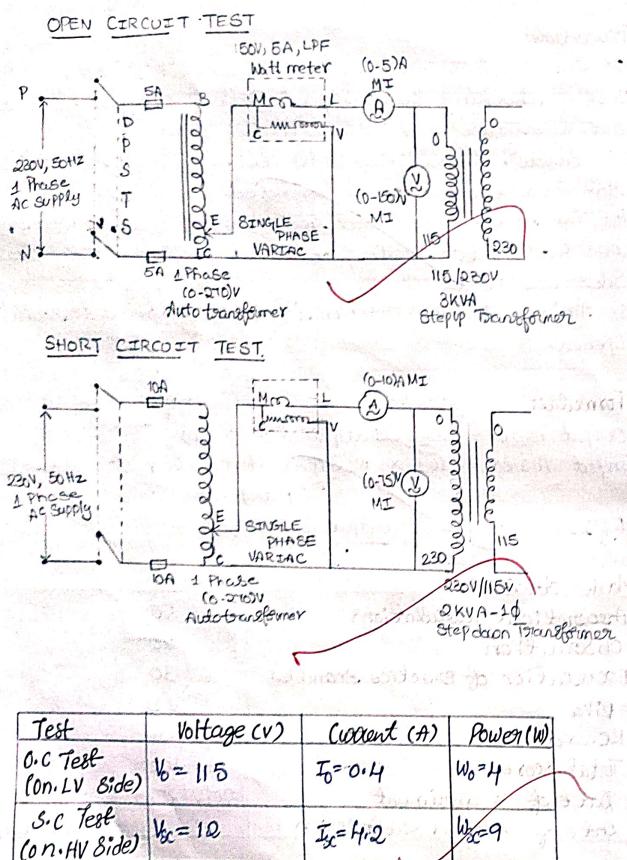**Result:** Thus the load test on Single phase transformer and efficiency and percentage regulation were calculated.



20/2/25

**Expt 10: OC and SC test on single phase transformer**

**Object:** To conduct load test on single phase transformer

**Apparatus Required**

S.NO	APPARATUS	RANGE	TYPE	QUANTITY
1	Ammeter	(0-10)A (0-5A)	HIMI	1, 1
2	Voltmeter	(0-150)V (0-300)V	MIMI	1, 1
3	Voltmeter	(230V, 5A) (115V, 5A)	LPF, HPF	1, 1
4.	Auto transformer	10A (0-260)V	-	1
5.	Resistive load	5kΩ, 230V	-	1
6.	Connecting wires	2.5 mm², copper	Copper	few

**Precautions:**

1. Auto Transformer should be in minimum position
2. The A.c supply is given and removed from the transformer under no load condition.

**Name plate Details:**

- KVA Rating
- Rated H.V Side Voltage - 230
- Rated H.V Side Current - 5A
- Rated L.V Side Voltage - 115V
- Rated L.V Side Current - 10A

**Fuse Rating Calculations:**

The required fuse ratings for O.C are 20% of rated current on L.V Side =  $(20/100) \times \text{Rated Current on L.V Side}$

The required fuse ratings for S.C are 120% of rated current on H.V Side =  $(120/100) \times \text{Rated current on H.V Side}$

**Procedure:****(I) O.C. TEST**

1. The circuit connections are made as per the circuit diagram.
2. Keeping the H.V. Winding open and the auto transformer in its minimum position the main Supply is switched ON.
3. By slowly and carefully adjusting the auto transformer, the rated Voltage (115V) is applied to L.V. Winding of the transformer.
4. Under this condition the ammeter ( $I_0$ ), Voltmeter ( $V_0$ ) and Wattmeter ( $W_0$ ) readings are noted down.
5. After the experiment is completed, the auto transformer is slowly brought back to minimum position and then the main Supply is switched off.

**(II) S.C. TEST**

1. The circuit connections are made as per the circuit diagram.
2. Short circuiting the LV winding and keeping the auto transformer in its minimum position, the main Supply is switched ON.
3. By slowly and carefully adjusting the auto transformer the rated current (which is calculated as H.V current rating \*  $1000 / \text{H.V}$  is circulated through the H.V winding).
4. Under this condition, the ammeter ( $I_{SC}$ ), the Voltmeter ( $V_{SC}$ ) and the Wattmeter ( $W_{SC}$ ) readings are noted down.
5. After the experiment is completed, the auto transformer is brought back to its minimum position and main Supply is switched OFF.

**MODEL CALCULATIONS**

1. To obtain the equivalent circuit parameters w.r.t H.V side
  - (i) From the O.C test the; constant loss Iron loss is noted  
 $W_C = W_0 = 4$  Watts
  - (ii) From the S.C test full load copper loss is noted  
 $W_{CU} = W_{SC} = 9$  Watts

For a transformer, the equivalent circuit parameters can be determined either w.r.t H.V side or L.V side. If the parameters are estimated on the L.V side; the resulting equivalent circuit is called H.V side Equivalent circuit of the transformer.

From the o.c test  $R_0$  and  $X_0$  are calculated using the following expressions,

$$R_0 \text{ (L.V)} = V_0 / I_{W0} = 115 / 0.398 \text{ ohms} = 289 \text{ k ohms}$$

$$X_0 \text{ (L.V)} = V_0 / I_{m0} = 115 / 0.398 \text{ ohms} = 289 \text{ ohms}$$

$$\text{Where } I_{W0} = I_0 \cos\theta = 0.4 \times \cos(85.09) = 0.084 \text{ A}$$

$$I_m = I_0 \sin\theta = 0.4 \times \sin(85.09) \text{ and } \theta = \cos^{-1}[V_0/V_0 I_0] = \cos^{-1}(0.084)$$

Since these values are calculated wrt L.V side (because o.c test is conducted on the L.V side), the equivalent values of ' $R_0$ ' and ' $X_0$ ' as referred to H.V side are determined as

$$R_0 \text{ (H.V)} = R_0 \text{ (L.V)} / k^2 = 289 / 4 = 72.25 \Omega$$

$$X_0 \text{ (H.V)} = X_0 \text{ (L.V)} / k^2 = 289 / 4 = 72.25 \Omega$$

Where,  $k = (\text{Secondary Voltage}) / (\text{Primary Voltage})$

$$= 115 / 230 \text{ for a step down operation}$$

$$= 230 / 115 \text{ for a step up operation}$$

Since we are assuming a step down operation  $k = 115 / 230 = 0.5$

$$R_T \text{ (H.V)} = W_{sc} / I_{sc}^2 = 9 / 4 \cdot 2^2 = 0.51 \Omega$$

$$Z_T \text{ (H.V)} = V_{sc} / I_{sc} = 12 / 4 \cdot 2 = 1.5 \Omega$$

$$X_T \text{ (H.V)} = [Z_T^2 \text{ (H.V)} - R_T^2 \text{ (H.V)}]^{1/2} =$$

$R_T \text{ (H.V)}$  and  $X_T \text{ (H.V)}$  are the total equivalent resistance and reactance of the transformer as referred to the H.V side whose values are

Calculated from the S.C test. Now the H.V side equivalent circuit is drawn.

### 2. To Pre-determine The Efficiency:

The percentage efficiency is then predetermined for different load conditions for a specified load power factor using the expression,

$$\% \text{ Efficiency} = \frac{x * KVA * \cos \phi * 1000}{(x * KVA * \cos \phi * 1000) + W_0 + x^2 WF \cdot L}$$

When  $x$  is the fraction of the full load which is 0.25 for 25% load, 0.5 for 50% load, 0.75 for 75% load, 1.0 for full load and 1.25 for 125% load and  $\cos \phi = 0.8$  the load P.F (Usually assumed as 0.8 lag). The efficiency values so calculated are entered in the tabular column as shown. A graph is plotted between percentage efficiency and the output as shown in model graph.

### 3. To pre-determine the percentage Regulation:

The regulation on full load for different leading and lagging power factors are predetermined by formula,

$$\% \text{ Regulation} = \frac{[I_T(H.V) * R_T(H.V) \cos \phi] + [I_T(H.V) * X_T(H.V) \sin \phi]}{V(H.V)} \%$$

Where + for lagging power factor, - for leading power factor

$I_{H.V}$  = Rated current on H.V side,  $V_{H.V}$  = Rated Voltage on H.V Side.

By assuming different leading and lagging power factor such as 0.2, 0.4, 0.6, 0.8 and 1.0 the regulation of the transformer for full load are determined and tabulated as shown below.

## Marks Obtained

Theoretical Calculations	20	20
Observation	20	20
Execution of Practice Examples	30	30
Viva	10	8
Record	20	20
Total Score	100	98
Date of Experiment	20/2/25	Jay
Date of Record Submission		Faculty Signature

## Result:-

Thus the O.C and S.C tests are conducted on the single phase efficiency Transformer.

20/2/23

## Expt. No. 11. Load test on a Single Phase Induction Motor

Aims: To conduct load test on single phase induction motor to plot the following performance characteristics

- 1) Output power Vs Efficiency
- 2) Output power Vs Speed
- 3) Input power Vs % Slip
- 4) Output Power Vs Torque
- 5) Output Power Vs Line current

## Apparatus Required

S.No	APPARATUS	RANGE	TYPE	QUANTITY
1	Ammeter	(0-20)A	MI	1
2	Voltmeter	(0-300)V	MI	1
3	Wattmeter	(300V, 10A)	MPF	1
4	Auto Transformer	(0, (0-270)V	-	1
5	Connecting Wires	2.5 Sq. mm	Copper	Few


## Fuse rating calculations:

For the load test the required fuse ratings are 120% of motor rated current

$$\text{Fuse Rating (current)} = (125/100) \times \text{Rated current}$$

## Precautions:

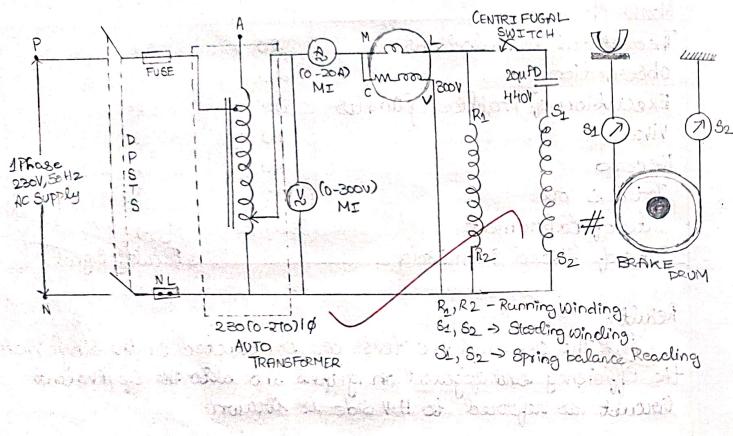
1. Remove the fuse carriers before wiring and start wiring as per the circuit diagram.
2. Check the position of the rheostat as specified.
3. The load on motor must be released initially.
4. Fuse Calculations: For load test the required fuse ratings are 120% of the rated current of the motor



S.NO	Line Voltage (V.L)	Line Current (I.L)	Input Power (W)	Spring Balance			Torque (N-m)	Speed (r.p.m.)	Output Power (W)	$\eta$ %	S %
				S1 (kg)	S2 (kg)	S1-S2 (kg)					
1.	220	2.1	240	0.7	0	0.7	0.65	1430	98	41	0.7
2.	220	3	500	1.4	3.2	1.8	1.67	1410	247	49	2
3.	220	3.5	620	3	5.4	2.4	2.23	1390	325	52	3
4.	220	4	760	3.2	7.3	4.1	3.82	1370	560	72	5
5.	220	4.5	940	4	8.5	4.5	4.19	1350	594	63	6

$N_s = 1440 \text{ r.p.m.}$

### MODEL GRAPH:

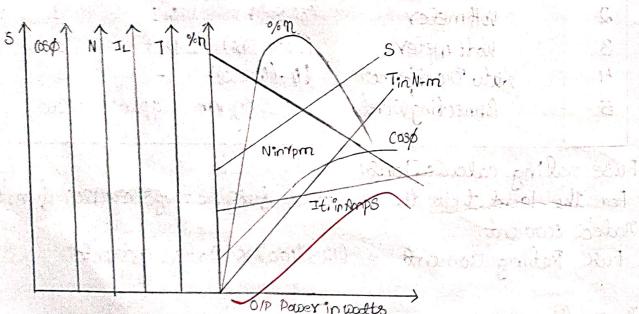

5. Replace the fuse carriers with appropriate fuse wires after the circuit connections are checked by the Staff in Charge.

### Procedure

1. The circuit connections are made as per the circuit diagram.
2. Keeping the motor field rheostat in its minimum position and the starter in its OFF position the main supply is switched on to the circuit.
3. The motor is started using the three point starter by slowly and carefully moving the starter handle from its off to on position.
4. The motor is brought to its rated speed by gradually adjusting the field rheostat and checked with the help of a tachometer.
5. Under this no load condition one set of readings namely, applied voltage ( $V_L$ ), line current ( $I_L$ ), the two spring balance readings ( $S_1$  and  $S_2$ ) and motor speed ( $r.p.m.$ ) are noted down in the tabular column.
6. The load on the motor is increased in steps gradually and at each step, all the meter readings and the motor speed are recorded in the tabular column. The above procedure is repeated until the motor is loaded to 120% of its rated current.
7. After the experiment is completed, the load on motor is gradually decreased to minimum and the rheostat is brought back to its original position and then the main supply is switched off.
8. Plot the performance characteristics.

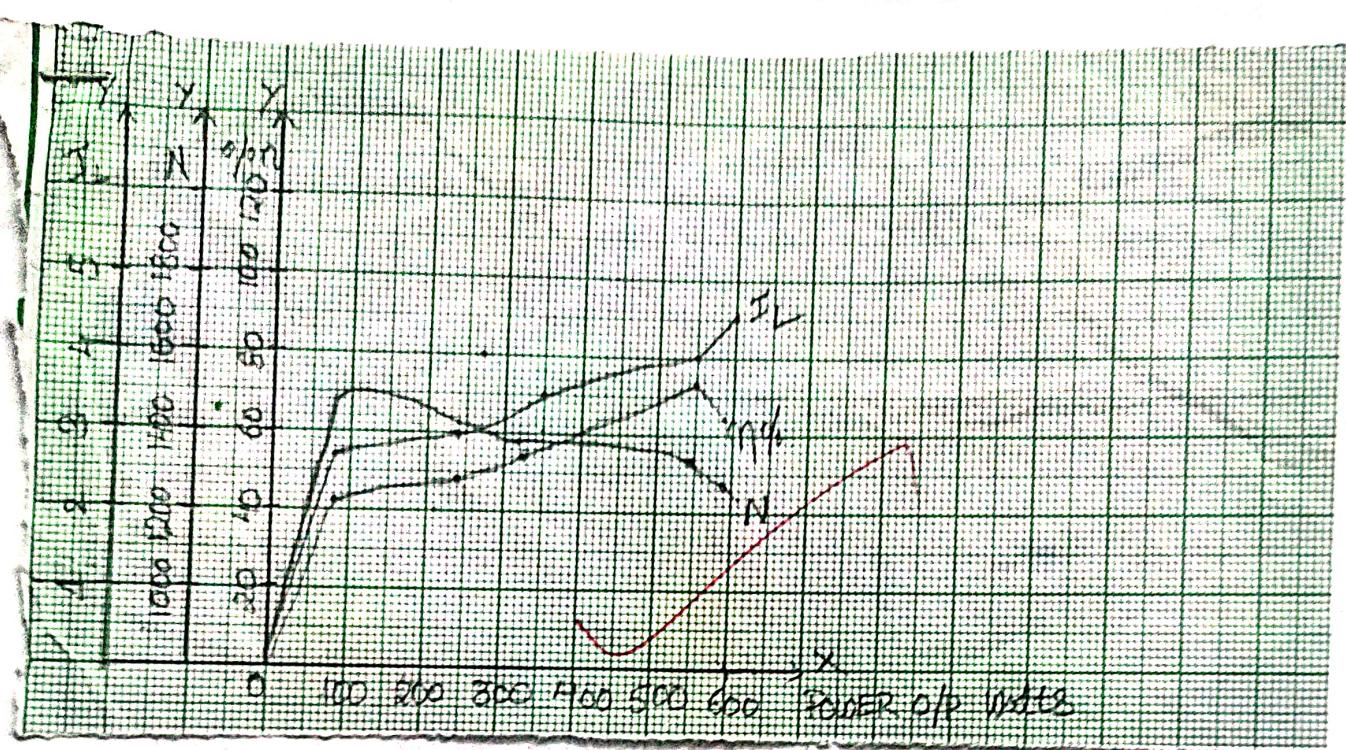


Abbildung 1: Die Abhängigkeit von der Frequenz bei gleichem Leistungsaufwand für zwei unterschiedliche Materialien und die Grenzfrequenz

## Model Calculations:

The circumference of the brake drum is measured and the radius of the drum is calculated using the expression

$$r = C / 2\pi$$

$$R = r + t/2$$

r - Radius of the Brake drum (cm)

C - Circumference of the Brake drum (cm)

R - Effective Radius (cm)

t - Thickness of the belt

The torque developed by the motor is given by

~~$$T = (S_1 - S_2) * R * 9.81$$~~

The output power of the motor is

~~$$P_{out} = \frac{2\pi N T}{60}$$~~

The efficiency of the motor

~~$$\eta = (P_{out} / P_{in}) * 100$$~~

The % slip of the motor


~~$$\% s = (N_s - N / N_s) * 100$$~~

~~$$N_s - \text{Synchronous Speed} = (120 \times f) / P$$~~

Marks obtained

Theoretical Calculations	20	20
Observation	20	20
Execution of Practice Examples	30	30
Viva	10	2
Record	20	20
Total Score	100	97
Date of Experiment	20/2/25	<del>20/2/25</del>
Date of record submission		Faculty Signature

~~Result:- Thus the load test on Single phase Induction motor is conducted and their performance characteristics are plotted.~~

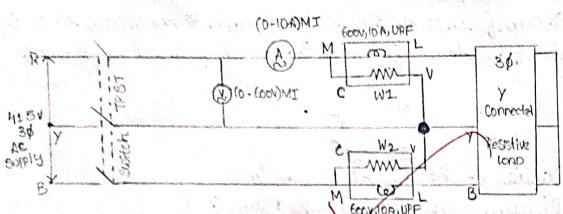CIRCUIT DIAGRAM

S.NO	Line Voltage (VL)	Line Current (IL)	Watt meter (W1)	Watt meter (W2)	$W = W1 + W2$	Calculated Power (W)
1.	400	2	140	680	0	680
2.	400	3.6	840	1200	50	200
3.	400	4.2	400	1600	10	280
4.	400	4.7	450	1800	100	400
					2200	2187.953

8/1/2/25

## Expt. No. 12. Three Phase Power Measurement Using Two Wattmeter method

Aim: To measure the power in three phase balanced Star-connected load using Wattmeter method.

## Apparatus Required:

S.NO	APPARATUS	RANGE	TYPE	QUANTITY
1	Ammeter	(0-10)A	MI	1
2	Voltmeter	(0-600)V	MI	1
3	Watt meter	(600, 10A)	LPF	2
4	Auto transformer	3φ, (0-600)V	-	1
5	Lamp load	-	-	1
6	Connecting wires	2.5 Sq. mm	Copper	Few

## Procedure:

1. Make the connections as per the circuit diagram shown in Figure.
2. Switch ON 3 phase AC Supply.
3. Apply load and measure the values of watt meters, ammeter and Voltmeter.
4. Switch off all the loads and supply.


## Model Calculations

1. Total power,  $P = W_1 + W_2$  Watts
2. Power Factor  $\cos \phi = \cos [\tan^{-1} \frac{S}{\sqrt{3}} (W_1 - W_2) / (W_1 + W_2)]^{\circ}$
3. calculated Power =  $\sqrt{3} V_L I_L \cos \phi$

Marks obtained			
Theoretical calculations	20	20	
Observation	20	20	
Execution of Practice Examples	30	30	
Viva	10	8	
Record	20	2	
Total Score	100	98	
Date of Experiment	21/2/25		Jeddy
Date of record Submission			Faculty Signature

## Result:

Thus the power in three phase balanced star connected load using two wattmeter method is measured and calculated.

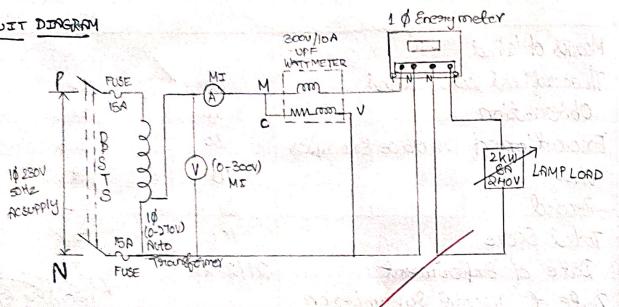CIRCUIT DIAGRAMTABULAR COLUMN

S.No	Line Voltage $V_L$ (V)	Line Current $I_L$ (A)	Time taken for 2 revolutions (Sec)	No. of revolutions (n)	Calculated Energy (Whr)	Measured Energy (Whr)
1	230	1.5	89	5	$3.73 \times 10^{-3}$	$3.33 \times 10^{-3}$
2	230	2.1	21	5	$2.8 \times 10^{-3}$	$3.33 \times 10^{-3}$

Meter Constant = 3600

Calculated Energy

$$\textcircled{1} \quad CE = \frac{V \times I \times t}{3600} = \frac{230 \times 1.5 \times 89}{3600} = 3.73 \times 10^{-3}$$

$$\textcircled{2} \quad CE = \frac{230 \times 2.1 \times 21}{3600} = 2.8 \times 10^{-3}$$

2/2/25

## Expt. No. 13. Energy consumption measurement using a Single Phase Energy meter

Aim: To measure the energy consumption using single phase Energy meter

Apparatus Required:-

S.No	APPARATUS	RANGE	TYPE	QUANTITY
1	Ammeter	(0-20)A	MI	1
2	Voltmeter	(0-300)V	MI	1
3	Auto transformer	16, (0-270)V	-	1
4	Lamp load	-	-	1
5	Connecting Wires	2.5 Sq. mm	Copper	Few

Procedure:-

1. Connect the circuit as shown in circuit diagram.
2. Connect the load rheostat 10 & 12 A in series with load.
3. Keep the variac in minimum output voltage position.
4. Keep the load in maximum position.
5. Adjust the variac output equal to the rated voltage of Energy meter.
6. Adjust the load till rated current of Energy meter passes through it.
7. Note down the time taken for 2 revolutions of disc in the Energy meter. Switch off the supply.
8. Note down the Voltmeter and ammeter readings.
9. Switch off the supply.
10. Repeat the above steps for different currents.

Model Calculations:

1. Calculated Energy Consumed during 'n' revolutions  $W_a = V^* I^* t / 3600$

= (Watt-hour)

Where,  $V$  = Voltage (v)

$I$  = Current (A)

$t$  = time (s)

2. Measured Energy by Energy meter  $WR = n / \text{meter constant}$

Marks obtained:

Theoretical Calculations	20	20
Observation	20	20
Execution of Practice Examples	30	30
Viva	10	8
Record	20	20
Total Score	100	98
Date of Experiment		
Date of record Submission		

Faculty Signature

Result:

Thus the Energy consumption using Single Phase Energy meter is measured.

## Expt. No. 14 Load Test on DC Shunt motor

**Aim:**

- To conduct load test on DC Shunt motor and to determine the efficiency using mechanical loading arrangement
- To draw the following characteristics curves
- Torque VS Armature current (Electrical characteristics)
- Speed VS Armature current (Electrical characteristics)
- Speed VS Torque (Mechanical characteristics)
- Performance curve

**Apparatus Required:**


SI.NO	NAME	SPECIFICATION	QUANTITY
1	DC Shunt motor, with spring balance load	2HP, 1440RPM, 230V 18. 1A	1 no
2	Voltmeter	(0-300)V, PMMC	1 no
3	Ammeter	(0-20)A, PMMC	1 no
4.	Rheostat	1250Ω, 0.8 A	1 no
5.	Tachometer	Digital type	1 no
6.	Connecting wires	PVC insulated COPPER	AS PER Required

**Precautions:**

- DC Shunt motor should be started and stopped under no load condition
- Field rheostat should be kept in the minimum position.
- Brake drum should be cooled with water when it is under load.

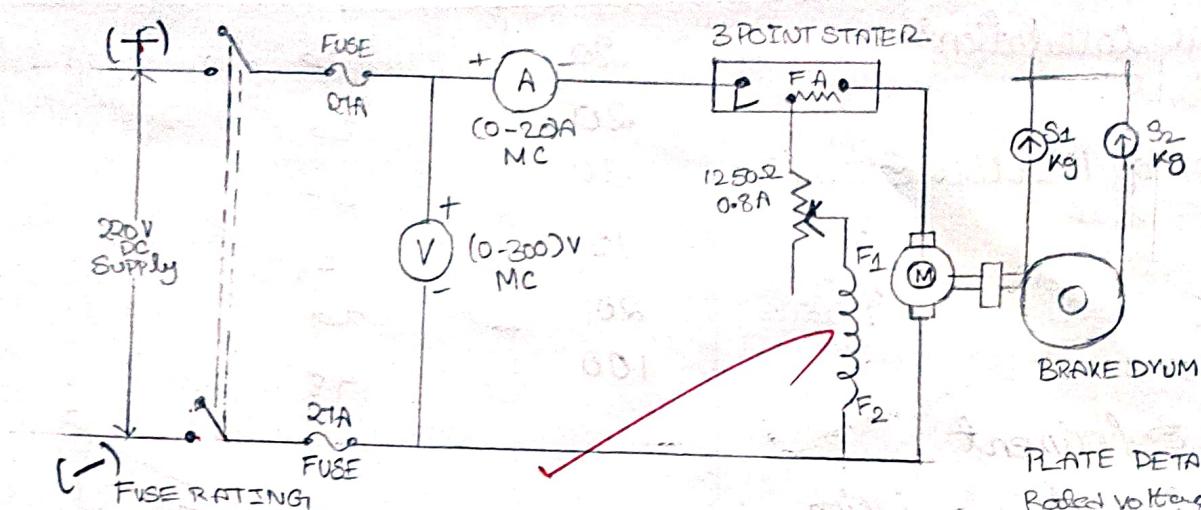**Procedure**

- Connections are made up as per the circuit diagram
- After checking the no load condition and minimum field rheostat position shunter resistance is gradually removed



FUSE RATING,  
125% rated current  
 $\frac{125 \times 21}{100} = 26.25A$

#### PLATE DETAILS

Rated voltage: 220V  
Rated current: 2A  
Rated Power: 3.5kW  
Rated speed: 1500 RPM

S.NO	Input Voltage (V) in Volts	Armature Current (I) in Amps	Speed (N) in RPM	W <sub>1</sub> in Kg	W <sub>2</sub> in Kg	W = (W <sub>2</sub> - W <sub>1</sub> ) in	Torque (T) in N-m	Output Power (P <sub>o</sub> ) in Watts	Input Power (P <sub>i</sub> ) in Watts	% Efficiency
1.	219	1.4	1448	0	0	0	0	0	306.6	0
2.	219	2	1428	1	1	0	0	0	488	0
3.	219	4.8	1400	0.1	3.4	3.3	2.91	426.4	1051	41
4.	219	6	1379	0.4	5.6	5.2	4.6	664	1814	51

- The motor is brought to its rated speed by adjusting the field rheostat.
- Ammeter, Voltmeter readings speeds and spring balance readings are noted under no load condition
- The load is often added to the motor gradually and for each load, Voltmeter, ammeter, Spring Balance readings and Speed of the motor are noted (Take readings up to rated current of the machine).
- The motor is then brought to no load condition and field rheostat to minimum position then switch off the supply.

Formulae used

$$\bullet \text{Torque } (T) = 9.81 (S_1 - S_2) \cdot r$$

Where,  $S_1, S_2 \rightarrow$  Spring balance readings in kg  
 $r \rightarrow$  Radius of brake drum in m

$9.81 \rightarrow$  Constant to convert kg to Newton

$$2. \text{ Output Power } (P_{out}) = 2\pi N T / 60$$

Where  $N =$  Speed in rpm

$$3. \text{ Input Power } (P_{in}) = V_L \cdot I_L \text{ Watts}$$

$V_L =$  Input Voltage in Volts

$I_L =$  Input Current in Amps

$$4. \% \text{ Efficiency} = (P_{out} / P_{in}) * 100$$

Date of record submission

Property signature

Result:

Thus, load test on DC Shunt motor is Experimentally Verified

### MODEL GRAPH

